

7 segment with adders


7 segment decoder

- 1 0 Collapse Duplicated Rows Show All Rows

16 of 16 rows shown

i_m3	i_m2	i_m1	i_m0	o_seg[7..0]
0	0	0	0	1 1 0 0 0 0 0 0
0	0	0	1	1 1 1 1 1 0 0 1
0	0	1	0	1 0 1 0 0 1 0 0
0	0	1	1	1 0 1 1 0 0 0 0
0	1	0	0	1 0 0 1 1 0 0 1
0	1	0	1	1 0 0 1 0 0 1 0
0	1	1	0	1 0 0 0 0 0 1 0
0	1	1	1	1 1 1 1 1 0 0 0
1	0	0	0	1 0 0 0 0 0 0 0
1	0	0	1	1 0 0 1 0 0 0 0
1	0	1	0	1 1 0 0 0 0 0 0
1	0	1	1	1 1 1 1 1 0 0 1
1	1	0	0	1 0 1 0 0 1 0 0
1	1	0	1	1 0 1 0 1 0 0 0
1	1	1	0	1 0 0 1 1 0 0 1
1	1	1	1	1 0 0 1 0 0 1 0

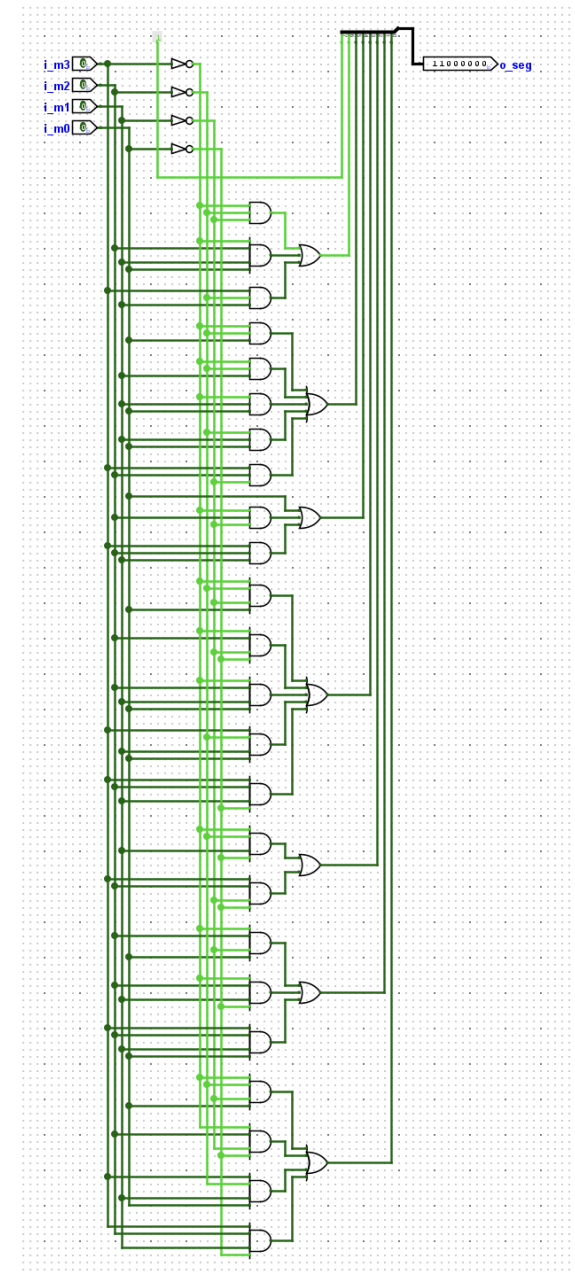Creating Truth Table – does 0-9 then repeats 0-5 past 9




Carry out truth table

- 1 0 Collapse Duplicated Rows Show All Rows

2 of 2 rows shown

z	s6	s5	s4	s3	s2	s1	s0
0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	1

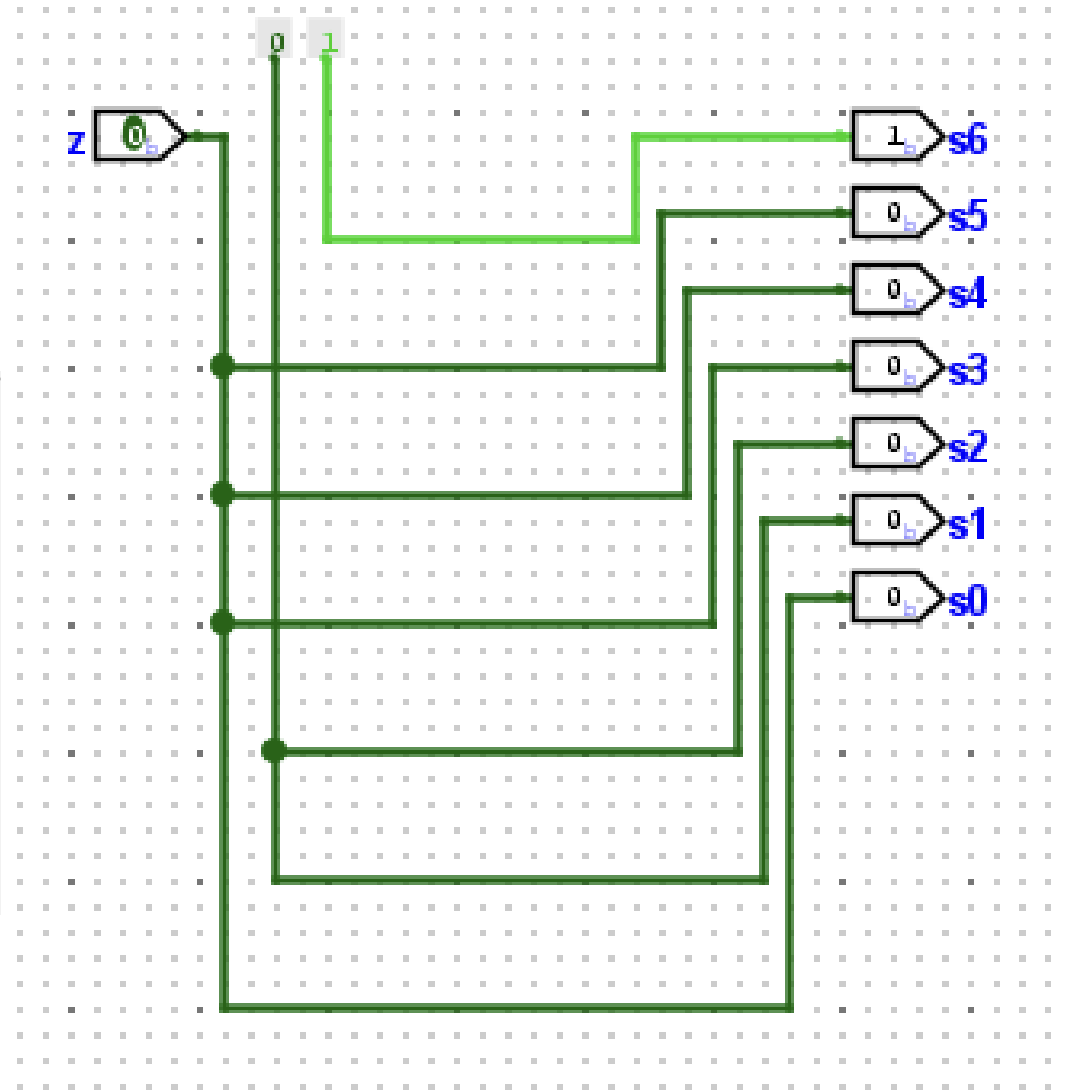


My comparator


- 1 0 Collapse Duplicated Rows Show All Rows

16 of 16 rows shown

v3	v2	v1	v0	z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

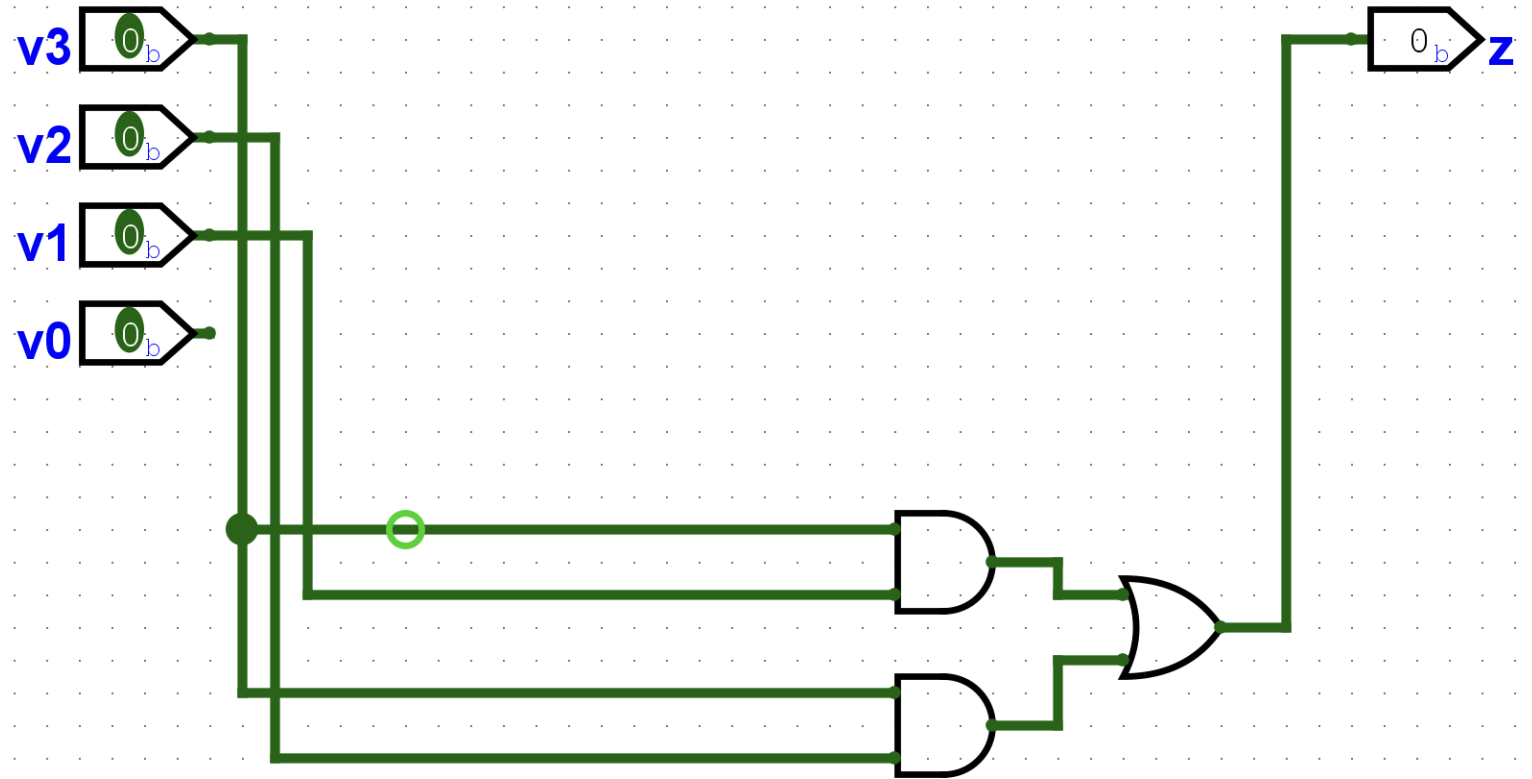

Putting it all together in Bin2Hex

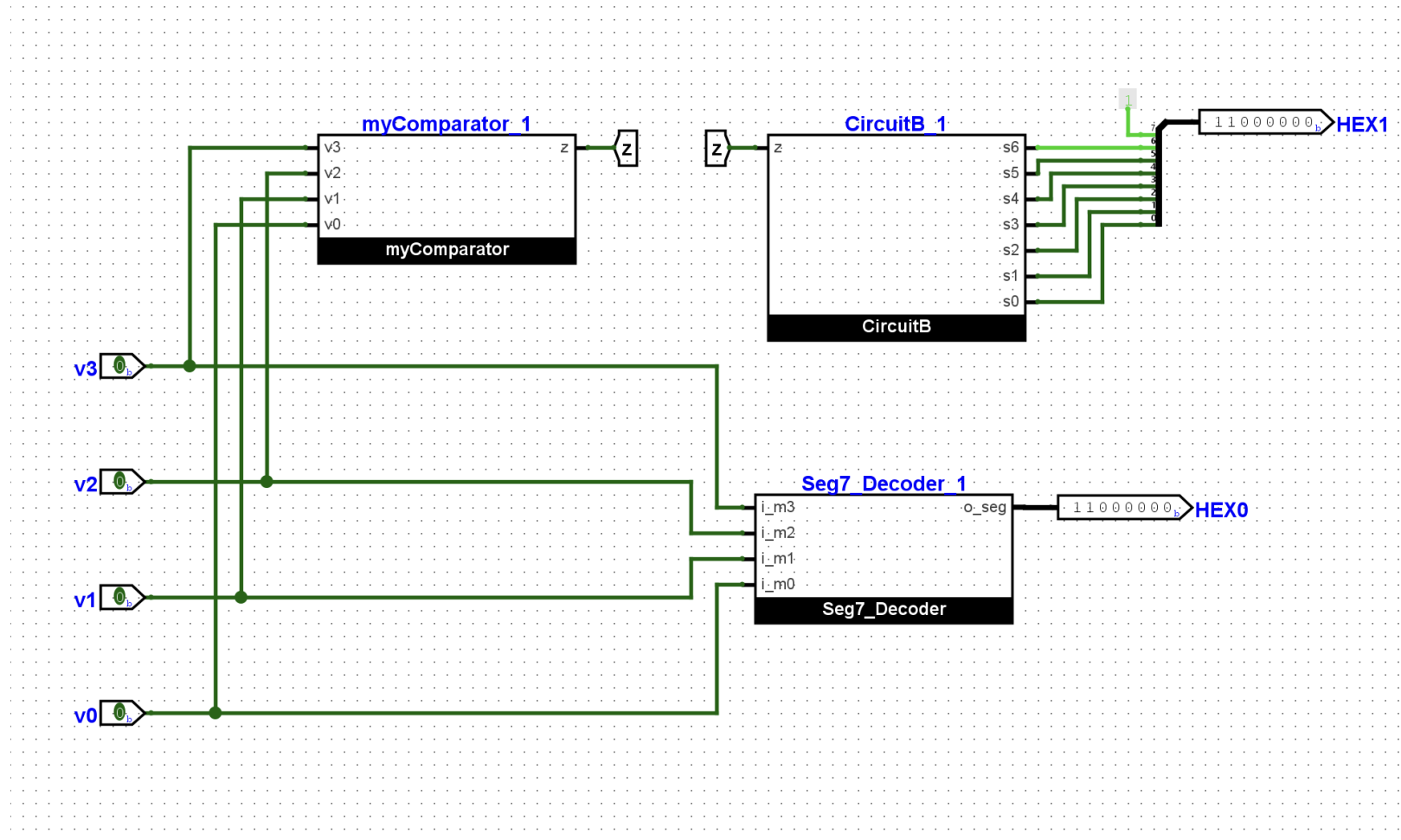

Working Circuit

