

Lab 5


Harrison Knight

Truth Table for Full Adder



8 of 8 rows shown

A	B	C	Sum	C_out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Circuit

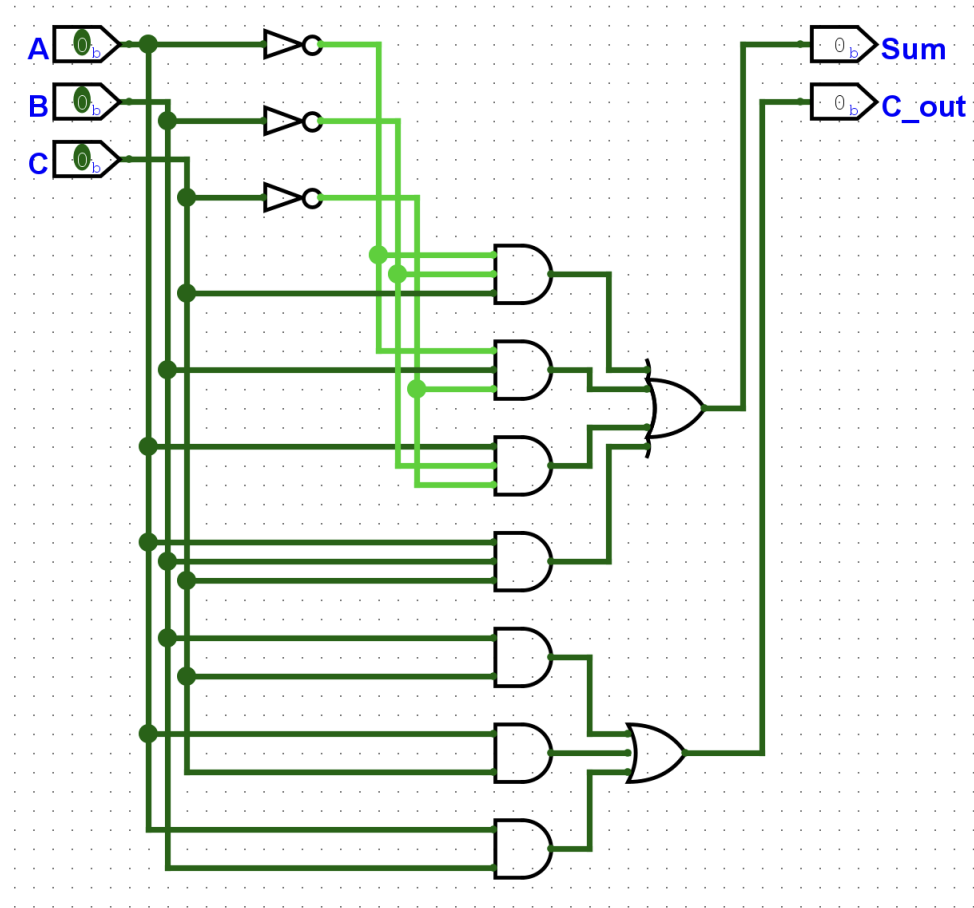

Mapping

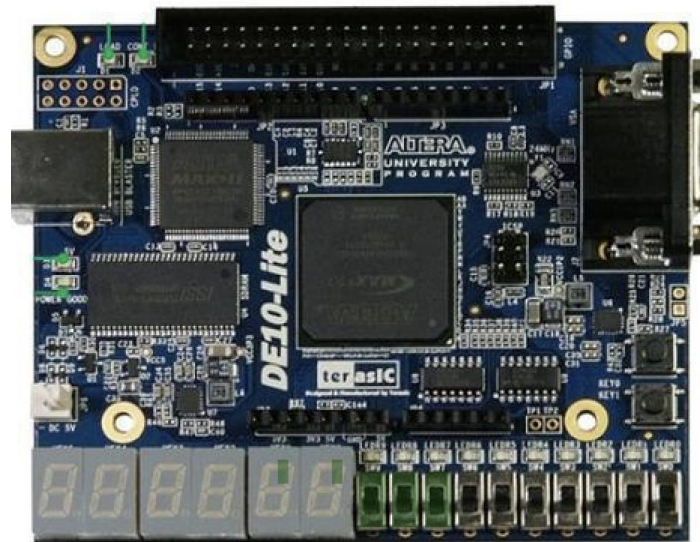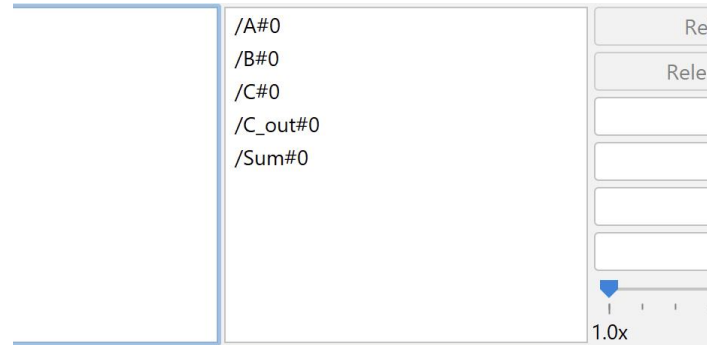

Sum	A	B	C
C_out			