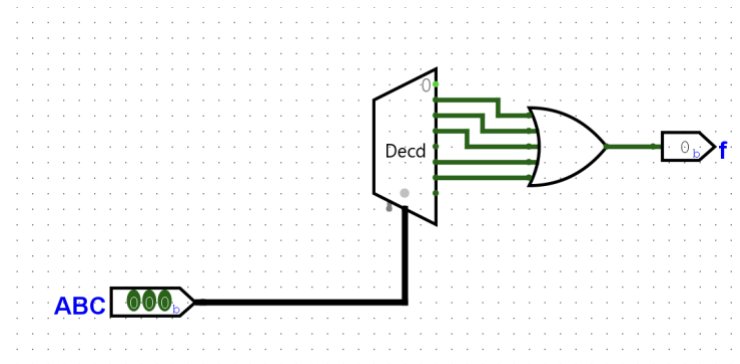


Question 1:

Truth Table

A	B	C	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Circuit:




Question 2:

Truth Table:

A	B	C	f	
0	0	0	1	
0	0	1	0	$B+C'$
0	1	0	1	
0	1	1	1	
1	0	0	0	
1	0	1	0	BC'
1	1	0	1	
1	1	1	0	


Circuit:

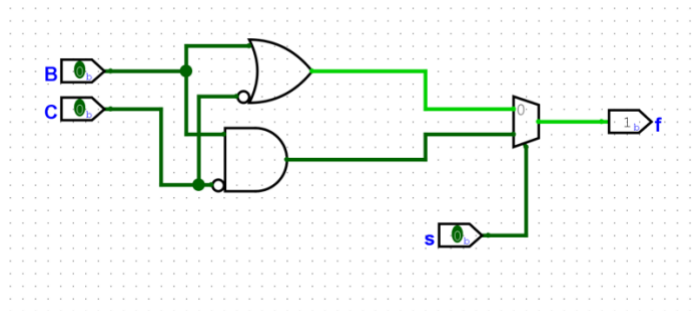

Question 3:

Truth Table:

A	B	C	f	
0	0	0	1	
0	0	1	0	$(B+C)'$
0	1	0	0	
0	1	1	0	
1	0	0	1	
1	0	1	0	$(B+C')$
1	1	0	1	
1	1	1	1	

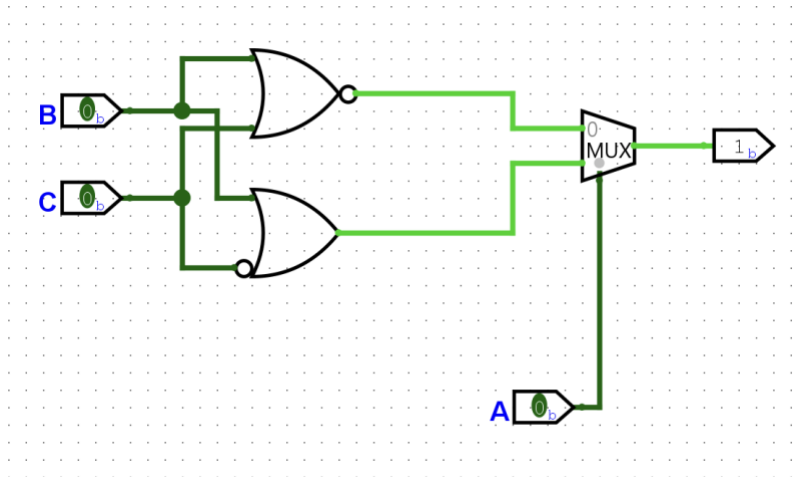


Question 4:

Truth Table:

A	B	C	f	
0	0	0	1	
0	0	1	0	$(B+C')$
0	1	0	1	
0	1	1	1	
1	0	0	0	
1	0	1	0	
1	1	0	1	(BC')
1	1	1	0	

Circuit:

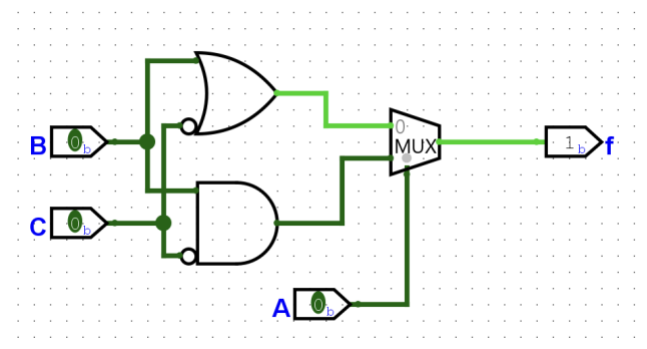


Question 5:

Truth Table: (4 to 1 on left, 2 to 1 on right) (^ symbol is a XOR)

A	B	C	f		
0	0	0	1		
0	0	1	1	1	
0	1	0	0		B'
0	1	1	0	0	
1	0	0	1		
1	0	1	0	C'	(B ^ C)'
1	1	0	0		
1	1	1	1	C	

4 to 1:

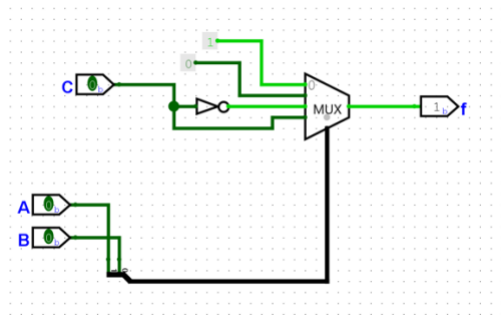

2 to 1 (Gate made with a MUX):

